
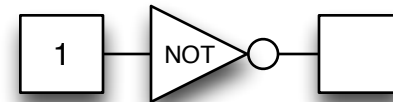


How Computers Work - Gate Rules





Name _____

Room _____

 NOT — Output the opposite value

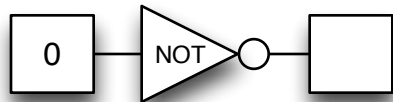

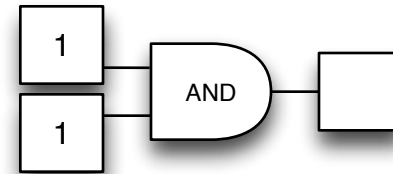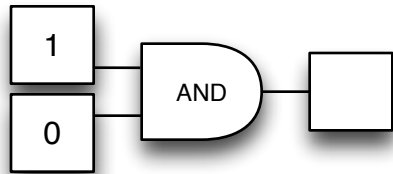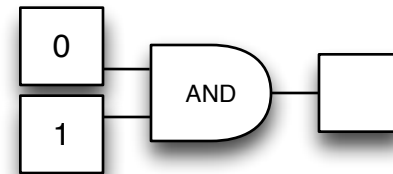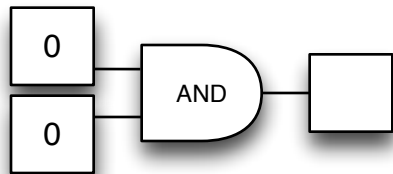 AND — Output 1 only if *both* inputs are 1



 OR — Output 1 if *any* input are 1

